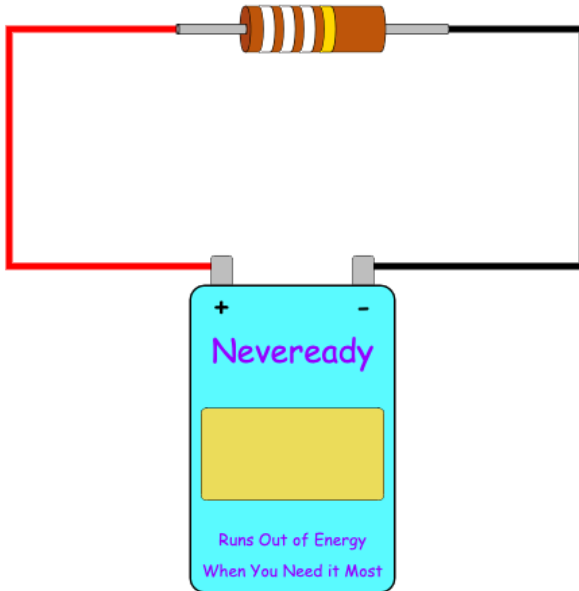


Finding Battery Power Simple

Step 1: Fill in the voltage of your battery and the colors of the stripes of your resistor



Step 2: Find the resistance of your resistor based on the color code. Show how you did this in the space below

Step 3: Neatly show your calculation for current flowing through your circuit

Step 4: Show your calculation for the power (energy per second) being supplied by your battery to the circuit. Enter your answers into your program to check that you did everything properly