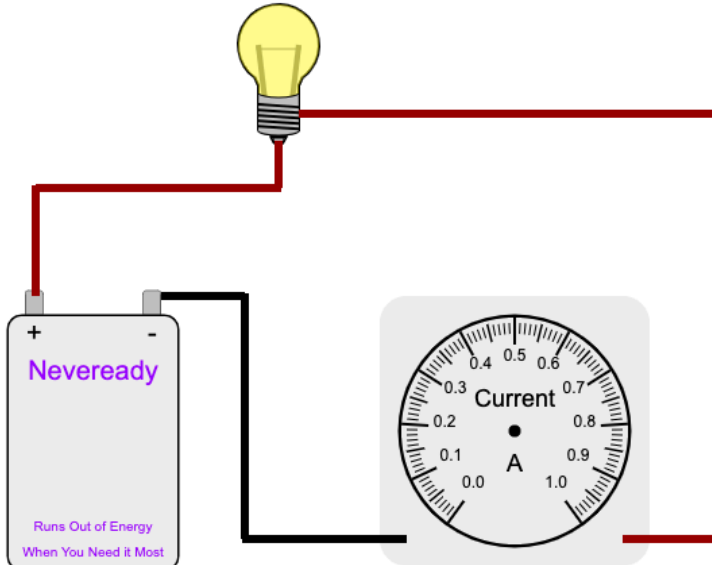


# Battery, Light, and Meter

Step 1: Fill in the voltage of your battery, the current being read by your meter and the time over which your circuit will be running.



Step 2: Neatly show your calculation for the power being used in the circuit.

Step 3: Neatly show your calculation of charge that flowed through the light bulb in the time indicated.

Step 4: Show your calculation of the energy that was converted in your bulb. Enter your answers into your program to check that you did everything properly